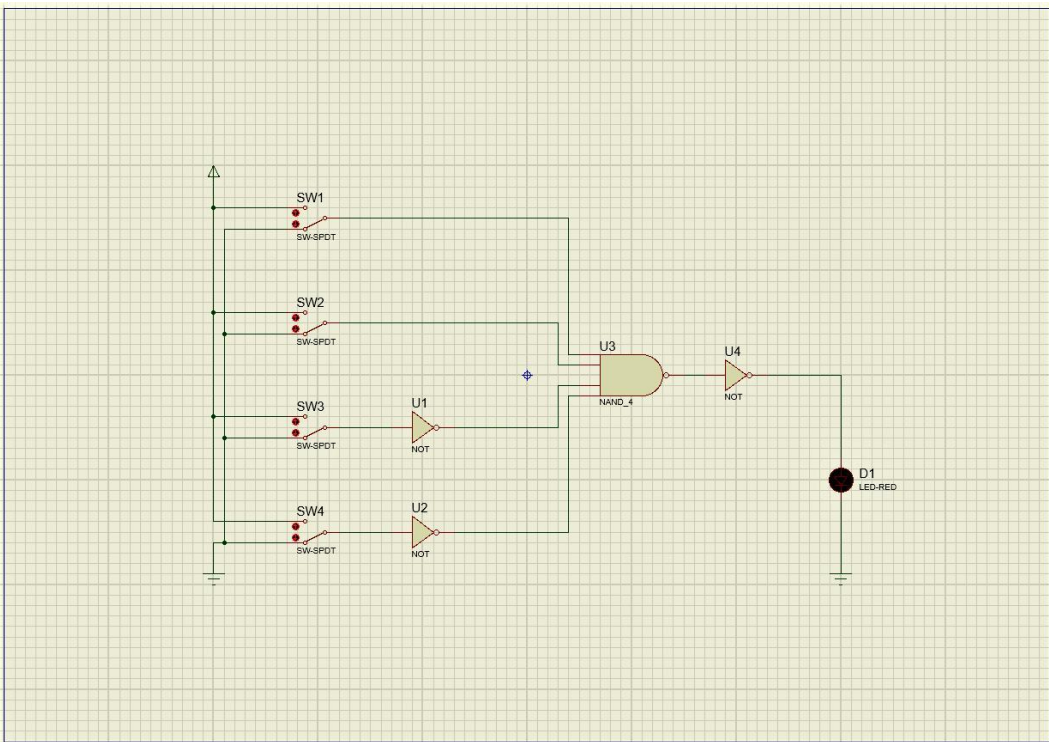


**INFORMATION TECHNOLOGY**  
**UNIVERSITY OF MUHAMMADIYAH SURAKARTA**  
**DIGITAL SYSTEMS**  
**9<sup>th</sup> PRACTICE**



**By:**  
**SUFYAN HABIB ZAINI**  
**NIM: L200184098**

# Experiment 1




Picture 1.1. Set of decoder

1. Column table

A	B	C	D	F
0	0	0	0	0
1	0	0	0	0
0	1	0	0	0
1	1	0	0	1
0	0	1	0	0
1	0	1	0	0
0	1	1	0	0
1	1	1	0	0
0	0	0	1	0
1	0	0	1	0
0	1	0	1	0
1	1	0	1	0
0	0	1	1	0
1	0	1	1	0
0	1	1	1	0
1	1	1	1	0


2. Decoder (F) only works (ON) when: A = 1, B = 1, C = 0, and D = 0.

3. Set of decoder that has output as a function:  $F = 1$ , if condition  $A = 0, B = 1, C = 1, D = 1$ . ( $F = A'BCD$ )

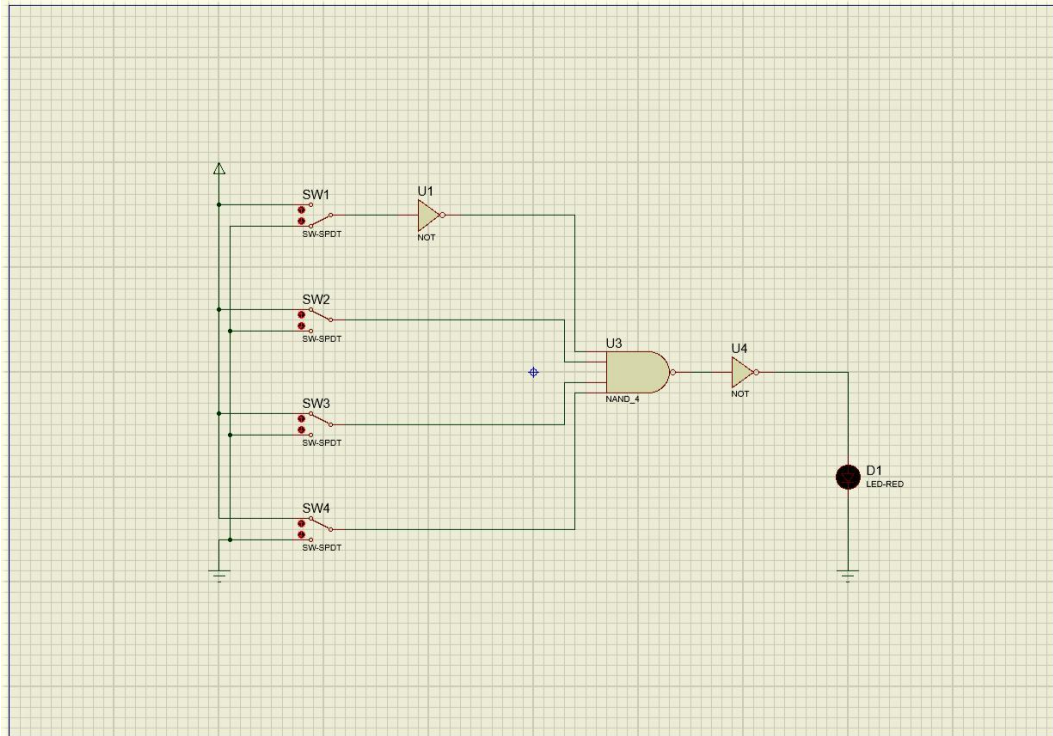

Picture 1.2. Set of decoder

## Experiment 2

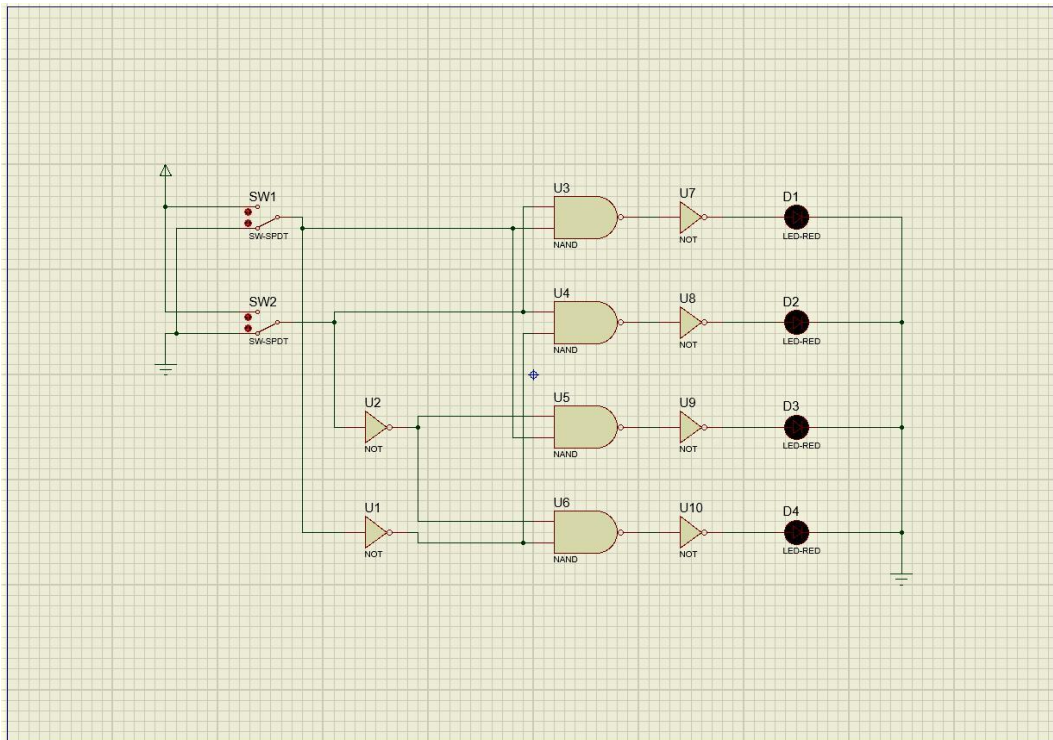

Picture 2.1. Logic gate combination


### 1. Column table

Input		Output LED			
SW1	SW2	D1	D2	D3	D4
0	0	0	0	0	1
0	1	0	1	0	0
1	0	0	0	1	0
1	1	1	0	0	0

### 2. Output result from the logic gate combination

- $D1 = SW1.SW2$
- $D2 = \overline{SW1}.SW2$
- $D3 = SW1.\overline{SW2}$
- $D4 = \overline{SW1}.\overline{SW2}$

### Experiment 3

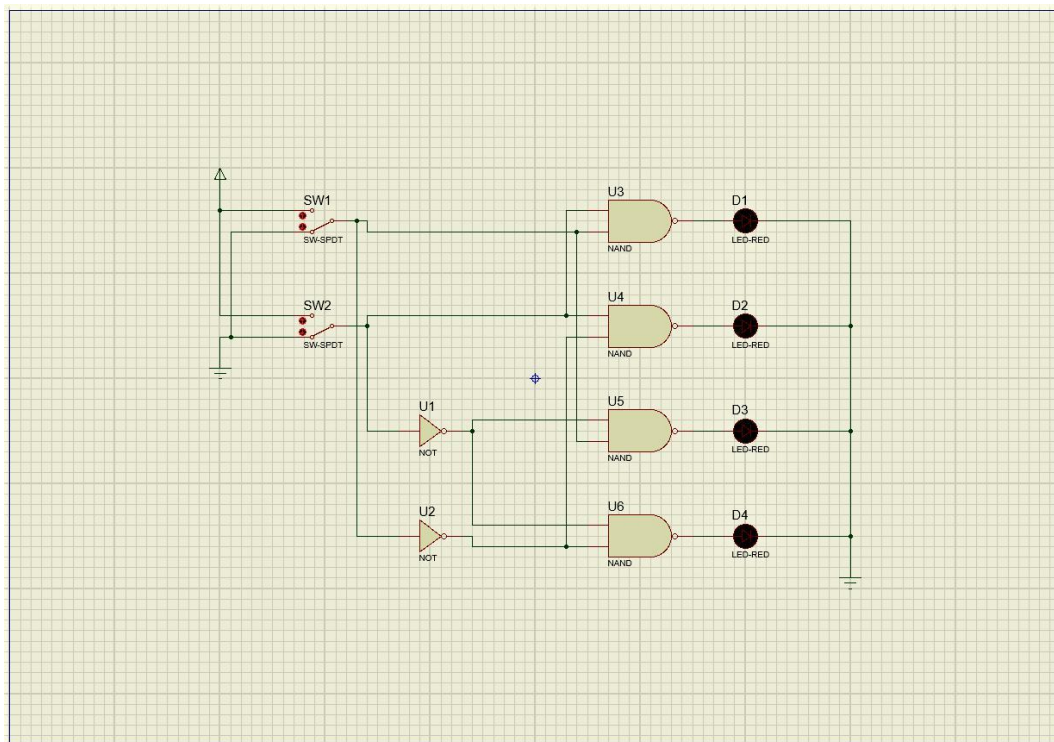

Picture 3.1. Logic gate combination

#### 1. Coloumn table

Input		Output LED			
SW1	SW2	D1	D2	D3	D4
0	0	1	1	1	0
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	1	1	1

#### 2. Output result from the logic gate combination


- $D1 = \overline{SW1} \cdot SW2$
- $D2 = \overline{SW1} \cdot \overline{SW2}$
- $D3 = SW1 \cdot \overline{SW2}$
- $D4 = SW1 \cdot SW2$

#### 3. Conclusion from experiment 2 and 3


in the second experiment there is a NOT gate located after the NAND gate, while in the third experiment there is no NOT gate located after the NAND gate. so the output results in experiments 2 and 3 are very different



Experiment 4

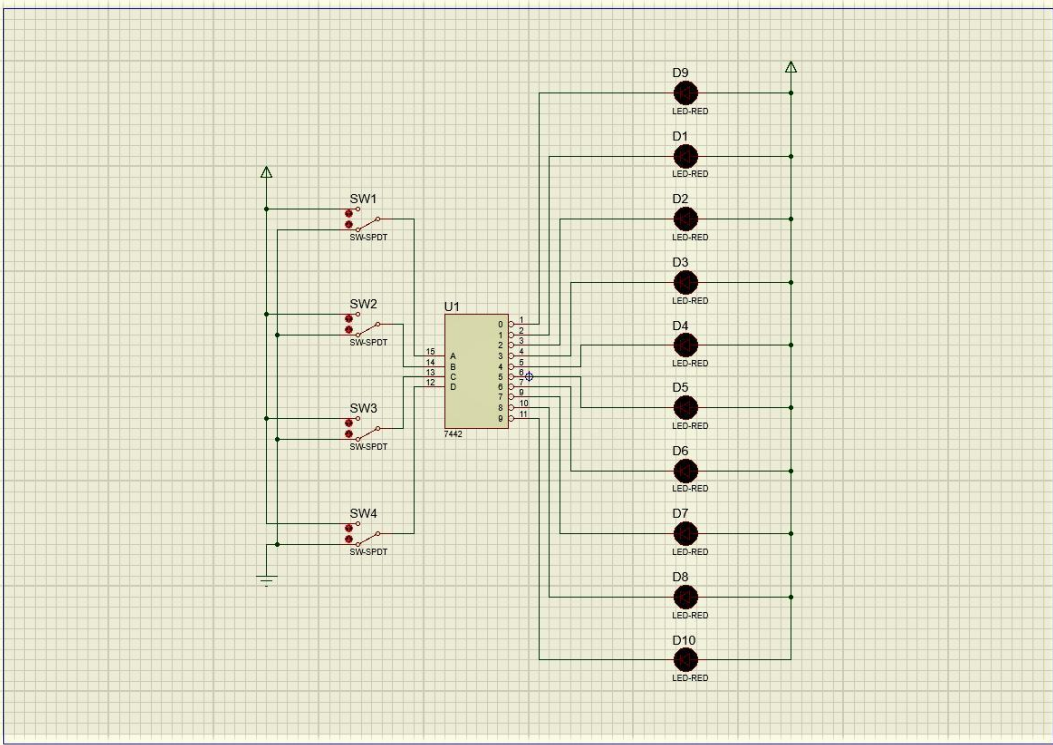

Picture 4.1. Common anode LED circuit

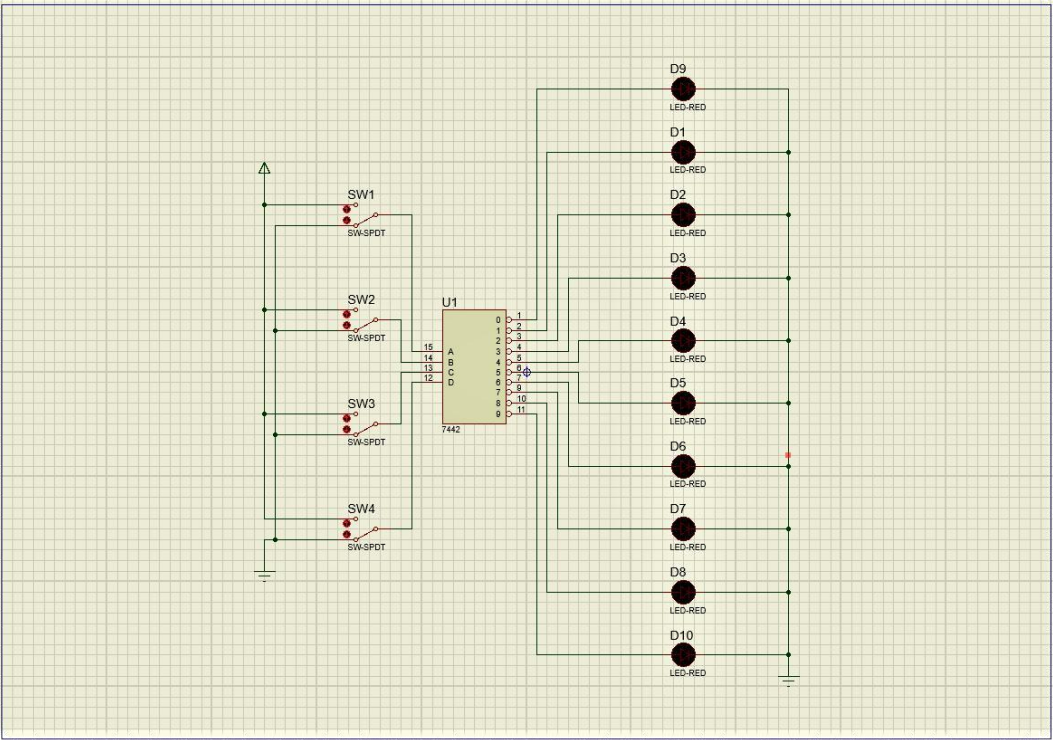

Picture 4.2. Common cathode LED circuit

## 1. Column table

a. Common anode LED

[illegible]

b. Common cathode LED

[illegible]